



قائمة الاسئلة

دوائر كهربائية 2 - كلية الهندسة - قسم الميكاترونكس - المستوى الثاني - 3 ساعات - درجة هذا الاختبار (50)


د. عادل راوع

- 1) Capacitive reactance is more when:
 - 1) - Capacitance is less and frequency of supply is more.
 - 2) Capacitance is less and frequency of supply is less.
 - 3) - Capacitance is more and frequency of supply is more.
 - 4) - Capacitance is more and frequency of supply is less.
- 2) Pure inductive circuit:
 - 1) - Consumes some power on average.
 - 2) - Does not take power at all from a line.
 - 3) Takes power from the line during some part of the cycle and then return back it during other part of the cycle.
 - 4) - None of the above.
- 3) In an RLC circuit, which of the following is always used as a vector reference?
 - 1) Voltage.
 - 2) - Resistance.
 - 3) - Impedance.
 - 4) - Current.
- 4) What is the unit of admittance?
 - 1) - ohm.
 - 2) - henry.
 - 3) - farad.
 - 4) ohm⁻¹
- 5) A sine wave a frequency of 50Hz, its angular frequency is _____ radian/second.
 - 1) 100π
 - 2) - 50π
 - 3) - 25π
 - 4) - 75π
- 6) The period of a sine wave is 0.02 seconds, its frequency is:
 - 1) - 100 HZ
 - 2) 50 HZ
 - 3) - 40 HZ
 - 4) - 20 HZ
- 7) A heater is rated as 230 V, 3 kW, A.C. The value 230 V refers to:
 - 1) - Average voltage.
 - 2) r.m.s. voltage.
 - 3) - Peak voltage.
 - 4) - none of the previous.
- 8)) If two sine waves of same frequency have a phase difference of pi radian, then:
 - 1) - both will reach their maximum values at same instant.
 - 2) - both will reach their minimum values at same instant.
 - 3) when one wave reaches its maximum value, the other will reach its minimum value.
 - 4) - none of the above.
- 9) The r.m.s. value and mean value is the same in the case of:
 - 1) - triangular wave.
 - 2) - half wave rectified sine wave.
 - 3) square wave.





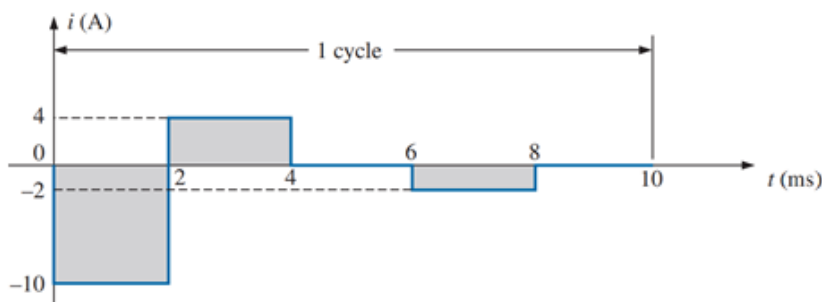- 4) - sine wave.
- 10) Power factor of an electrical circuit is equal to:
- 1) - R/Z .
 - 2) cosine of phase angle difference between current and voltage.
 - 3) - kW/kVA.
 - 4) - sine wave.
- 11) the time constant of an inductive circuit
- 1) Increases with increase of inductance and decrease of resistance.
 - 2) - Increases with increase of inductance and increase of resistance.
 - 3) - Increases with decrease of inductance and decrease of resistance.
 - 4) - Increases with decrease of inductance and increase of resistance.
- 12) In a highly capacitive circuit the:
- 1) - Apparent power is equal to active power.
 - 2) - Reactive power is more than to apparent power.
 - 3) Reactive power is more than to active power.
 - 4) - Active power is more than to reactive power.
- 13) Power factor of the following circuit will be unity:
- 1) - Inductance.
 - 2) - Capacitance.
 - 3) Resistance.
 - 4) - Both Inductance ,Capacitance
- 14) In a pure resistive circuit:
- 1) - The current lags behind the voltage by 90°
 - 2) - The current leads the voltage by 90°
 - 3) - The current can lag or lead the voltage by 90° .
 - 4) The current is in phase with voltage.
- 15) The input of an A.C. circuit having power factor of 0.8 lagging is 40 kVA, the power drawn by the circuit is:
- 1) - 12 kW.
 - 2) - 22 kW.
 - 3) 32 kW.
 - 4) - 64 kW.
- 16) as the next figure the average value of waveform is:



- 1) - -10 A.
 - 2) -1.6 A.
 - 3) - 4A
 - 4) - 0A
- 17)



The voltage across a 0.5 H coil is $v = 100 \sin(20t)$. Then the sinusoidal expression for the current is:

- a. $i = 10 \sin(20t - 90^\circ)$.
- b. $i = 10 \sin(20t + 90^\circ)$.
- c. $i = 10 \sin(20t)$.
- d. $i = 10 \sin(20t - 60^\circ)$.


- 1) a
- 2) b
- 3) c
- 4) d

18) With Conversion of the voltage-controlled source in next Figure to a current- controlled source $I = :$

- a. $0.48 A \angle 10^\circ$
- b. $4.82 A \angle 0^\circ$
- c. $0.48 A \angle 0^\circ$
- d. $0.40 A \angle 0^\circ$

- 1) a
- 2) b
- 3) c
- 4) d

19) from the next figure $I_2 = :$

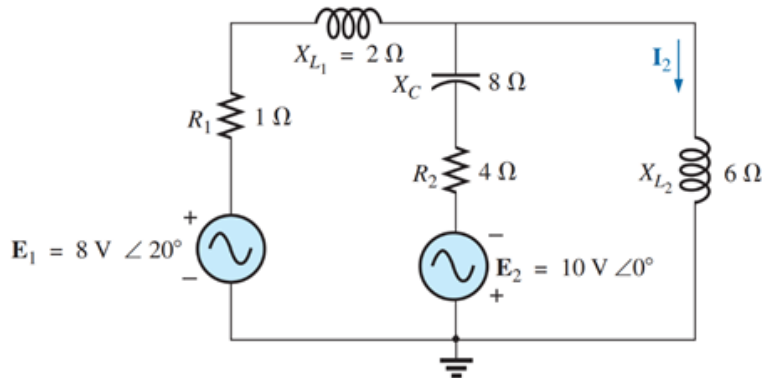


- 1) $-1.72 A \angle -86.92^\circ$.
- 2) $1.72 A \angle -86.92^\circ$.
- 3) $-1.27 A \angle -86.92^\circ$.
- 4) $1.27 A \angle -86.92^\circ$.

20)






from the next figure $Z_T =$:

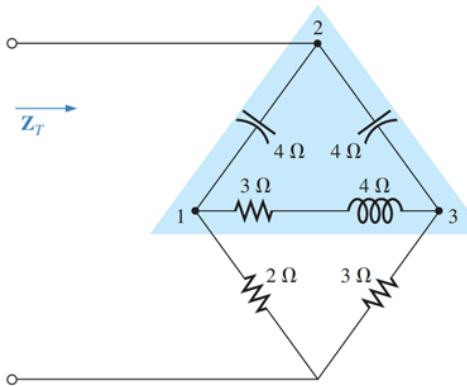

- 1) - $23.5 \Omega \angle - 58.41^\circ$.
- 2) - $2.35 \Omega \angle - 68.41^\circ$.
- 3) + $2.35 \Omega \angle - 58.41^\circ$.
- 4) - $3.25 \Omega \angle - 85.41^\circ$.

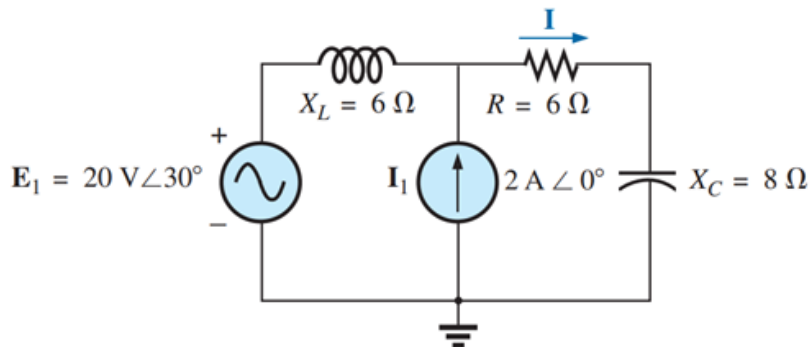21) from the next figure the current I through the 6Ω resistor is:




- 1) - $2.24 A \angle - 70.2^\circ$.
- 2) + $4.42 A \angle 70.2^\circ$.
- 3) - $44.2 A \angle 7.02^\circ$.
- 4) - $4.42 A \angle 60.2^\circ$.

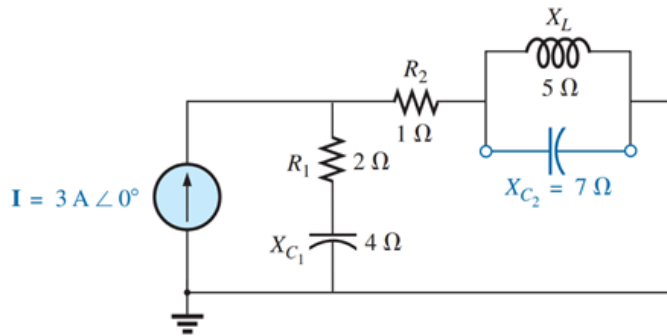22)






from the next figure the Norton equivalent circuit for the network external to the 7Ω capacitive reactance is:



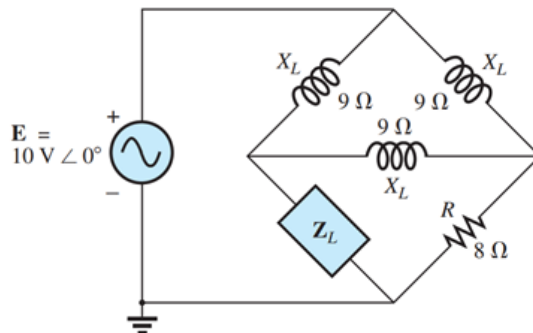- 1) $I_N = 2.68 \text{ A} \angle -10.3^\circ$. and $Z_N = 7.50 \Omega + j 2.50 \Omega$
 - 2) $I_N = 26.8 \text{ A} \angle -20.3^\circ$. and $Z_N = 7.50 \Omega + j 2.50 \Omega$
 - 3) $I_N = 2.68 \text{ A} \angle -10.3^\circ$. and $Z_N = 5.70 \Omega + j 25.0 \Omega$
 - 4) $I_N = 2.68 \text{ A} \angle -10.3^\circ$. and $Z_N = 2.50 \Omega + j 7.50 \Omega$
- 23) from the next figure the for maximum power delivering to the load the impedance Z_L must be:



- 1) $Z_L = -0.72 \Omega - j 5.46 \Omega$
- 2) $Z_L = 0.72 \Omega - j 5.46 \Omega$
- 3) $Z_L = 5.2 \Omega - j 3.6 \Omega$
- 4) $Z_L = 7.2 \Omega - j 54.6 \Omega$