



قائمة الاسئلة

اختبار النهائي للعام الجامعي 2025/2024 - كلية الهندسة :: دوائر كهربائية 2 - كلية الهندسة - قسم الطبية الحيوية - المستوى الثاني - 3 ساعات - در. م. ماجد علي

- 1) Which of the following factors can affect the shape of a sine wave?
 - 1) - Amplitude only
 - 2) - Frequency only
 - 3) + Both amplitude and frequency
 - 4) - None of the above
- 2) What is the correct mathematical expression for a sine wave if the RMS value is 7.07 V and the frequency is 50Hz?
 - 1) + $10 \sin (100\pi t)$
 - 2) - $10 \cos (2\pi * 50 t)$
 - 3) - $7.07 \sin (2\pi * 50 t)$
 - 4) - $7.07 \cos (2\pi t)$
- 3) If the frequency is 60 Hz and the wave starts at zero volts at 0° , what is the first time the wave will reach its peak value?
 - 1) - 1/120 seconds
 - 2) - 1/60 seconds
 - 3) - 1/100 seconds
 - 4) + 1/240 seconds
- 4) If the peak-to-peak voltage of a sine wave is 141.5 V, what is the RMS value of this wave?
 - 1) - 100 V
 - 2) - 70.75 V
 - 3) + 50 V
 - 4) - 200 V
- 5) If the distance between the capacitor plates is doubled, the capacitance will become:
 - 1) - Twice the original value
 - 2) + Half the original value
 - 3) - Remain unchanged
 - 4) - Equal to zero
- 6) Which of the following capacitors can withstand the highest voltage?
 - 1) + Ceramic capacitors
 - 2) - Electrolytic capacitors
 - 3) - Plastic-film capacitors
 - 4) - Thin-layer capacitors
- 7) An uncharged capacitor and a resistor are connected in series with a switch and a 12 V battery. At the instant the switch is closed, the voltage across the capacitor is
 - 1) - 12 V
 - 2) - 6 V
 - 3) - 24 V
 - 4) + 0 V
- 8) Why is an inductor often wound around a ferromagnetic core?
 - 1) - To reduce self-inductance
 - 2) + To increase inductance
 - 3) - To increase resistance
 - 4) - To minimize current variation
- 9) How do non-magnetic materials affect inductance?
 - 1) - Significantly increase it
 - 2) - Reduce it to zero





- 3) ☒ + Do not affect it
- 4) ☐ - Prevent magnetic field formation
- 10) Which of the following reduces parasitic capacitance in an inductor?
- 1) ☐ - Decreasing spacing between turns
- 2) ☐ - Using thicker wire
- 3) ☒ + Increasing spacing between turns
- 4) ☐ - Using a high-permeability core material
- 11) What determines the winding resistance in an inductor?
- 1) ☐ - Only the number of turns
- 2) ☒ + Wire material and length
- 3) ☐ - Magnetic flux density
- 4) ☐ - Core resistance
- 12) **An inductor and a resistor are in series with a sinusoidal voltage source. The frequency is set so that the inductive reactance is equal to the resistance. If the frequency is increased, then**
- a. $V_R > V_L$
- b. $V_L < V_R$
- c. $V_L = V_R$
- d. $V_L > V_R$
- 1) ☐ - a
- 2) ☐ - b
- 3) ☐ - c
- 4) ☒ + d
- 13) If resistance increases in a circuit with both resistance and capacitive reactance, the phase angle?
- 1) ☐ - Increases
- 2) ☒ + Decreases
- 3) ☐ - Remains the same
- 4) ☐ - Becomes 90°
- 14) The unit of true power is?
- 1) ☐ - VAR
- 2) ☒ + Watt (W)
- 3) ☐ - Volt-Ampere (VA)
- 4) ☐ - Ohm (Ω)
- 15) In an AC circuit where the phase angle between voltage and current increases, the power factor?
- 1) ☐ - Increases
- 2) ☐ - Remains constant
- 3) ☒ + Decreases
- 4) ☐ - Is always 1
- 16) In a certain series resonant circuit, $V_C = 150$ V, $V_L = 150$ V, and $V_R = 50$ V. The value of the source voltage is
- 1) ☐ - 150 V
- 2) ☐ - 300 V
- 3) ☒ + 50 V
- 4) ☐ - 350 V
- 17) At steady-state, the inductor acts as:
- 1) ☐ - An open circuit
- 2) ☐ - A variable resistor
- 3) ☐ - A fixed resistor
- 4) ☒ + Almost a short circuit





- 18) In an RL circuit where the final current is 10 A, what is the current in the coil after 5 tau?
- 1) - 8.5 A
 - 2) ☒ + 9.93 A
 - 3) - 6.3 A
 - 4) - 7.5 A
- 19) $(5\angle 45^\circ)(2\angle 20^\circ)$ is equal to
- a. $7\angle 65^\circ$
 - b. $10\angle 25^\circ$
 - c. $10\angle 65^\circ$
 - d. $7\angle 25^\circ$
- 1) - a
- 2) - b
- 3) ☒ + c
- 4) - d
- 20) In a series RC circuit, the voltage across the resistance is
- 1) - In phase with the source voltage
 - 2) - Lagging the source voltage by 90°
 - 3) ☒ + In phase with the current
 - 4) - Lagging the current by 90°
- 21) In a parallel RL circuit, there are 2 mA rms in the resistive branch and 2 mA rms in the inductive branch. The total rms current is
- 1) - 4 mA
 - 2) - 5.66 mA
 - 3) - 2 mA
 - 4) ☒ + 2.83 mA
- 22) The power factor in a series RLC circuit at resonance is?
- 1) - 0
 - 2) ☒ + 1
 - 3) - Dependent on R
 - 4) - Dependent on L and C
- 23) The total reactance of a series RLC circuit at resonance is
- 1) ☒ + zero
 - 2) - equal to the resistance
 - 3) - infinity
 - 4) - capacitive
- 24) In a series RLC circuit, if inductive reactance is greater than capacitive reactance, the phase angle is?
- 1) ☒ + Positive
 - 2) - Negative
 - 3) - Zero
 - 4) - Depends on R only
- 25) A Thevenin ac equivalent circuit always consists of an equivalent ac voltage source and an equivalent
- 1) - Capacitive reactance
 - 2) - Inductive reactance
 - 3) ☒ + Series impedance
 - 4) - Parallel impedance
- 26) When can the superposition theorem be applied in multi-source circuits?
- 1) - When frequencies are different






- 2) ☒ + When frequencies are the same
- 3) ☐ - Only in DC circuits
- 4) ☐ - When all sources are pure resistances
- 27) A Norton ac equivalent circuit always consists of an equivalent
- 1) ☐ - ac current source in series with an equivalent impedance
- 2) ☐ - ac current source in parallel with an equivalent reactance
- 3) ☒ + ac current source in parallel with an equivalent impedance
- 4) ☐ - ac voltage source in parallel with an equivalent impedance
- 28) To maximize coupling between two coils, they are:
- 1) ☐ - Reduced in turns for the second coil
- 2) ☐ - Supplied with lower AC frequency
- 3) ☒ + Wound on a common core
- 4) ☐ - Spaced farther apart
- 29) A transformer is used for
- 1) ☐ - dc voltages
- 2) ☒ + ac voltages
- 3) ☐ - both dc and ac
- 30) **In the isolated transformers**
- a) $V_{Pri} > V_{Sec}$
- b) $V_{Pri} < V_{Sec}$
- c) $V_{Pri} = V_{Sec}$
- d) $V_{Pri} \leq V_{Sec}$
- 1) ☐ - a
- 2) ☐ - b
- 3) ☒ + c
- 4) ☐ - d
- 31) If the primary winding = 100 turns & secondary winding = 400 turns, then the turn ratio (n) equals
- 1) ☐ - 1/4
- 2) ☐ - 200
- 3) ☐ - 400
- 4) ☒ + 4
- 32) The primary winding of a transformer has 120 V AC across it. What is the secondary voltage if the turns ratio is 5?
- 1) ☐ - 24
- 2) ☒ + 600
- 3) ☐ - 60
- 4) ☐ - 240
- 33) If the voltage on the primary winding of the transformer is 10 V DC, then the voltage of the secondary winding is:
- 1) ☐ - 10 V
- 2) ☒ + 0 V
- 3) ☐ - Depends on the turn's ratio
- 4) ☐ - More than 10 V
- 34) If 10 W of power are applied to the primary of an ideal transformer with a turn's ratio of 5, the power delivered to the secondary load is
- 1) ☐ - 50 W
- 2) ☐ - 0.5 W





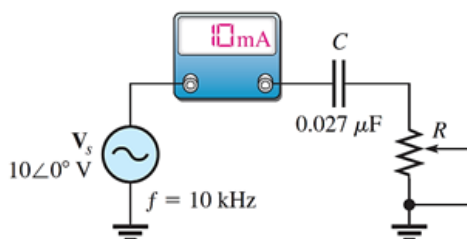- 3) - 0 W
4) ☒ + 10 W
- 35) When a three-phase generator is used instead of a single-phase generator, the required copper wire size:
1) - Increases
2) ☒ + Decreases
3) - Remains constant
4) - Depends on frequency
- 36) Which of the following applications benefits most from constant load power?
1) - Solar power systems
2) ☒ + Heavy induction motors
3) - Precision electronic circuits
4) - Fluorescent lamps
- 37) In a three-phase system, the voltages are separated by
1) - 90°
2) - 30°
3) - 180°
4) ☒ + 120°
- 38) The phase current produced by a certain 240 V, Y-connected generator is 12 A. The corresponding line current is
1) - 36 A
2) - 4.0 A
3) ☒ + 12 A
4) - 6.0 A
- 39) A certain Δ -connected generator produces phase voltages of 30 V. The magnitude of the line voltages is
1) - 10 V
2) ☒ + 30 V
3) - 90 V
4) - none of these
- 40) **To decrease the phase angle below 45° , the following condition must exist:**
a) $R = X_C$
b) $R < X_C$
c) $R > X_C$
d) $R = 10X_C$
- 1) - a
2) - b
3) ☒ + c
4) - d
- 41) **To what value must the rheostat be set in Figure (1) to make the total current 10 mA?**



Page

Figure (1)


- 1) - 1 k Ω






- 2) ☒ + 807.8 Ω
- 3) ☐ - 500 Ω
- 4) ☐ - 900 Ω

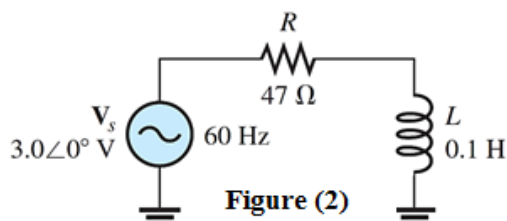42) Determine θ for the circuit in Figure (2):



- 1) ☐ - 51.3°
- 2) ☐ - 45°
- 3) ☐ - 83.7°
- 4) ☒ + 38.7°

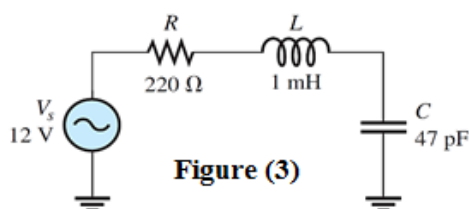43) Find the resonant frequency in Figure (3):




Page 9 of 10

- 1) ☒ + 734.1 KHz
- 2) ☐ - 734.1 Hz
- 3) ☐ - 23.2 KHz
- 4) ☐ - 23.2 Hz

44) For the circuit in Figure (4), find the total currents in polar form.

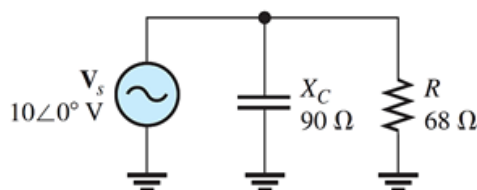- a) $I_{tot} = 18 \angle 37.1^\circ$ mA
- b) $I_{tot} = 184 \angle 70^\circ$ mA
- c) $I_{tot} = 184 \angle 37.1^\circ$ mA
- d) $I_{tot} = 1.8 \angle 37.1^\circ$ mA



- 1) ☐ - a
- 2) ☐ - b
- 3) ☒ + c
- 4) ☐ - d


45)





Find the impedance in Figure (5), and express it in polar form.

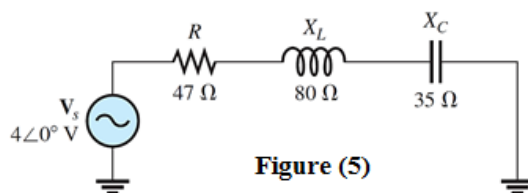- a) $65 \angle 43.8^\circ \Omega$
- b) $162 \angle 43.8^\circ \Omega$
- c) $65 \angle 46.3^\circ \Omega$
- d) $9.6 \angle 43.8^\circ \Omega$



- 1) ☒ a
- 2) ☐ b
- 3) ☐ c
- 4) ☐ d

