

1/13 الصفحة

## قائمة الاسئلة


ث ساعاد	المستوى الرابع - حاسبات- ثلا	صناعي- كلية الهندسة - قسم الكهرباء-	لجامعي 2025/2024م-كلية الهندسة :: تحكم م	اختبار النهائي للعام ا
				د. نعمان

- A \_\_\_\_ is an example of an actuator that could be controlled by a discrete output from a PLC.
  - a) pushbutton
  - b) motor starter
  - c) limit switch
  - d) all of the above
  - 1) a
  - 2) + t
  - 3) 0
  - 4) d
- 2) Field or real-world devices refer to
  - a) input devices only.
  - b) output devices only.
  - c) load devices only.
  - d) all devices that are physically wired to the PLC.
  - 1) a
  - 2) b
  - 3) c
  - 4) + d
- 3) The two methods of transmitting PLC digital data are
  - a) AC and DC.
  - b) input and output.
  - c) serial and parallel.
  - d) negative and positive
  - 1) a
  - 2) b
  - 3) + 0
  - 4) d

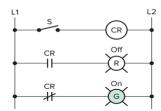
4)



In the hardwired relay control circuit shown, when the switch is closed, CR coil is:



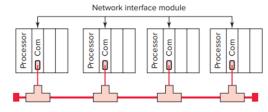- a) energized, the red light is off, and the green light is on.
- b) de-energized, the red light is off, and the green light is on.
- c) energized, the red light is on, and the green light is off.
- d) energized, and the red and green lights are both on.
- 1) a
- 2) b
- 3) + c
- 4) d
- 5) The type of network connection topology shown in Figure is



- a) bus.
- b) tree.
- c) star.
- d) ring.
- 1) + a
- 2) b
- 3) c
- 4) d
- 6) Network \_\_\_\_\_ defines how data are arranged and coded for transmission on a

network.

- a) devices
- b) protocol
- c) medium
- d) functions
- 1) a
- 2) + 1
- 3) c

d

7)




The fundamental job of a local area network (LAN) is to provide \_\_\_\_\_between devices.

- a) communication
- b) isolation
- c) connections
- d) protection
- 1) + a
- 2) t
- 3) -
- 4) 6
- 8) A distributive control system (DCS)
  - a) permits the distribution of the processing task among several controllers.
  - b) always utilizes a single large computer.
  - c) will stop the whole process if one control element fails.
  - d) is the least flexible type of control system.
  - 1) + a
  - 2) t
  - 3) 0
  - 4) d
  - PLC system data communications is accomplished using
    - a) network links.
    - b) point-to-point serial communications links.
    - c) transformer links.
    - d) both a and b
    - 1) 8
    - 2) b
    - 3) c
    - 4) + (
- 10) .The two types of patterns used to accomplish the scan function are:
  - a) up and down.
  - b) horizontal and vertical.
  - c) input and output.
  - d) left and right.
  - 1) a
  - 2) + b
  - 3) 0



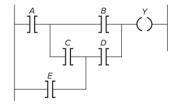- 4) d
- 11) Which hardware circuit is essential for safety in a PLC?
  - a) Latching Circuit.
  - b) Interlock Circuit.
  - c) Safety Digital Circuit.
  - d) Emergency Stop Circuit.
  - 1) a
  - 2) b
  - 3) 0
  - 4) + d
- 12) 12. Which one is the example of a device that could be used to provide a discrete input to a PLC?
  - a) Selector Switch
  - b) Pushbutton.
  - c) Limit Switch.
  - d) All of the options.
  - 1) a
  - 2) t
  - 3) c
  - 4) + d
- 13) Identify an example of a device that can be controlled by a discrete input to a PLC.
  - a) Motor Starter.
  - b) Selector Switch
  - c) lights
  - d) All of the options.
  - 1) a
  - 2) + b
  - 3) 0
  - 4) d
- $\begin{tabular}{ll} 14) & The Boolean equation for the logic represented in the ladder diagram can be expressed as: \\ \end{tabular}$




- a) Y = (AB) + (ACD) + (DE)
- b) Y = (AB) + (CD) + E
- c) Y = (AB) + (AC) + (AD) + (ED)
- d) Y = (AB) + (ACD) + (DE) + (BCE)



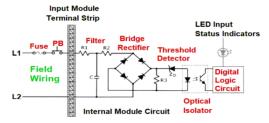
- 1) a
- 2) b
- 3) c
- 4) + d
- 15) What is the purpose of the Battery Backup in a PLC?
  - a) To Store User Programs
  - b) To Provide Emergency Power During a Power Loss
  - c) To Convert Signals
  - d) To Connect Network Devices
  - 1) a
  - 2) + b
  - 3) 0
  - 4) d
- 16) . What is the most common form of memory used to store, back up, or transfer PLC programs?
  - a) RAM.
  - b) Flash EEPROM.
  - c) EEPROM.
  - d) Both Flash EEPROM and EEPROM.
    - 1) a
  - 2) b
  - 3) c
  - 4) + (
- 17) What does the I/O system in a PLC provide an interface between?
  - a) Input modules and output modules.
  - b) The CPU and field equipment.
  - c) The CPU and I/O rack.
  - d) The I/O rack and I/O modules.
  - 1) a
  - 2) + b
  - 3) 0
  - 4) d



What is the purpose of the zener diode (ZD) in the schematic diagram?



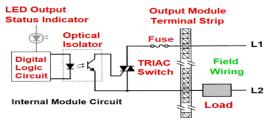- a) Assist in diagnosing faults.
- b) Define the minimum detectable voltage level.
- c) Provide protection against electrical noise interference.
- d) Segregate logic circuits from higher line voltage.
- 1) a 2) + b
- 3) c
- 4) d
- 19) Where does the input signal to the module originate from?



- a) The input field device.
- b) The output field device.
- c) Internal logic circuitry of the processor.
- d) Either the input field device or output field device.
- 1) a
- 2) b
- 3) + c
- 4) d
- 20) What is the purpose when the PLC system is used with an Interposing Relay?
  - a) Isolate the load from the controller.
  - b) Control a high resistance.
  - c) Control a high current load.
  - d) Vary the speed of a motor.
  - 1) a
  - 2) b
  - 3) + 0
  - 4) d
- 21)




One function of a PLC input interface module is to:

- a) accept signals from field devices and convert them into signals that can be used by the processor.
- b) convert signals from the processing unit into values that can be used to control the machine or process.
- c) input signals from the programming device and convert them into signals that can be used by the CPU.
- d) interpret and execute the user program that controls the machine or process
- 1) + a
- 2) b
- 3) c
- 4) d
- 22) What are the typical variances for analog inputs and outputs?
  - a) 0 to 20 mA.
  - b) 4 to 20 mA.
  - c) 0 to 10 volts.
  - d) All of the options.
  - 1) a
  - 2) t
  - 3) 0
  - (4) + d
- 23) A current sourcing sensor is connected to which type of PLC input module?
  - a) Current sinking.
  - b) Current sourcing.
  - c) Alternating current.
  - d) Either current sinking or sourcing.
  - 1) + a
  - 2) b
  - 3) 0
  - 4) d



24. For the block diagram of the output module shown in Figure, the input comes from

the

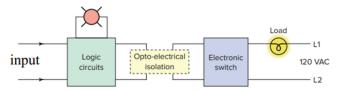

- a) input field device.
- b) processor.
- c) output field device.
- d) line power supply.
- 1) \_ a
- 2) + 1
- 3) -
- 4) d

The main element of an analog output module is:

- a) AC to DC rectifier.
- b) DC to AC inverter.
- c) Analog to digital converter.
- d) Digital to analog converter.
- 1) a
- 2) t
- 3) \_ \_ 0
- $\cancel{\Lambda}$  +  $\cancel{A}$
- 26) What type of PLC is typically used for small-scale applications?
  - a) Modular PLC.
  - b) Specialized PLC.
  - c) Redundant PLC.
  - d) Compact PLC.
  - 1) a
  - 2) b
  - 3) \_ c
  - 4) + d




What ensures that a PLC can recover its program after a power failure?

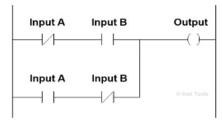- a) RAM.
- b) EEPROM.
- c) CPU.
- d) ROM.
- 1) \_ a
- 2) + b
- 3) c 4) - d
- 28) What specification in a PLC system defines the number of field inputs or outputs that can be connected to a single module?
  - a) Electrical isolation.
  - b) Points per module.
  - c) Threshold voltage.
  - d) Current per input.
    - 1) a
    - 2) +
    - 3) 0
    - 4) d
- The ladder logic in PLC consists of \_\_\_\_\_
  - a. Logic gates
  - b. Functional blocks
  - c. Relay contacts and coils
  - d. Relays
  - 1) a
  - 2) b
  - 3) + c
  - *a*) *d*



What is the specific logic gate function depicted by PLC ladder logic?



- a) XOR.
- b) XNOR.
- c) NAND.
- d) NOR.
- 1) + a
- 2) 1
- 3) 0
- 4) d
- The relays operate on \_\_\_\_\_
  - a) Low power
  - b) Control circuits of very high power
  - c) Both a and b
  - d) None of the above
  - 1) a
  - 2) t
  - 3) + 0
  - 4) d
- 32) Discrete output modules with transistor outputs can be used for control of

..... devices.

- a) AC.
- b) DC.
- c) AC or DC.
- d) None of the above
- 1) a
- 2) + b
- 3) 0
- 4) 33)




A continuous process is

- a) one that never shuts down.
- b) used only for simple tasks.
- one in which raw materials enter one end of the system and the finished product comes out the other end.
- d) used only with computers
- 1) a
- 2) b
- 3) + 0
- 4) d
- 34) . Communication between different PLC architectures and protocols is \_\_\_\_\_ made possible by the use of
  - a) rectifiers.
  - b) gateways.
  - c) repeaters.
  - d) hubs.
  - 1) a
  - 2) + b
  - 3) 0
  - 4) d
- The output interface module connects to \_\_\_\_\_
  - a) sensing devices such as switches or pushbuttons.
  - b) load devices such as lamps or solenoids.
  - c) a programming device such as a computer.
  - d) all of the above
  - 1) \_ a
  - 2) + t
  - 3) 0
- Volatile memory elements can be classified as those that
  - a) do not retain stored information when the power is removed.
  - b) retain stored information when the power is removed.
  - c) do not require a battery backup.
  - d) both b and c.
  - 1) + a
  - 2) b



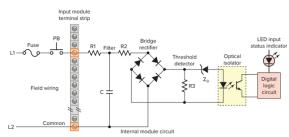- 3) c
- 4) d
- 37) A human machine interface (HMI) \_\_\_\_\_
  - a) allows the user to monitor a process.
  - b) allows the user to control a process.
  - c) can provide a graphical representation of a process.
  - d) all of the above
  - 1) a
  - 2) I
  - 3) 0
  - (4) + d
- 38) At the start of the PLC scan the \_\_\_\_\_
  - a) status of all inputs is read.
  - b) status of all outputs is updated.
  - c) program is executed.
  - d) diagnostics and communications tasks are executed.
  - 1) + a
  - 2) 1
  - 3) -
  - 4) d
- 39) The schematic diagram of Figure is that of a(n)



- a) discrete output module.
- b) discrete input module.
- c) analog output module.
- d) analog input module.
- 1) a
- 2) + b
- 4) d



When talking about PLC memory, 1K refers to \_\_\_\_\_ words.

- a) 255.
- b) 1124.
- c) 1024.
- d) 124
- 1) a
- 2) t
- 3) + c
- 4) d